

Roll No.....

Total No. of Sections : 03

Total No. of Printed Pages : 03

Code No. : C-193

Annual Examination - 2019

BCA Part - I

(BCA-101)

THEORETICAL FOUNDATION

OF COMPUTER SCIENCE

Paper – III

INTRODUCTORY ELECTRONICS

Max.Marks : 50

Time : 3 Hrs.

Min.Marks : 20

**Note :** Section 'A', containing 10 very short-answer-type questions, is compulsory. Section 'B' consists of short answer type questions and Section 'C' consists of long answer type questions. Section 'A' has to be solved first.

**Section - 'A'**

**Answer the following very short-answer-type questions in one or two sentences : (1 × 10=10)**

- Q.1 Define "Semiconductor".
- Q.2 What is P-type semiconductor?
- Q.3 Draw symbol for AND and Not gate.
- Q.4 Define Potential Barrier in a diode.
- Q.5 What is Gray Code?
- Q.6 Find  $(10.22)_{10} = (?)_2$

**P.T.O.**

(2)

Code No. : C-193

- Q.7 Draw symbol for NPN and PNP transistors.  
Q.8 Convert  $(999)_8$  into hexadecimal number.  
Q.9 Define Overflow.  
Q.10 What are types of ROM?

**Section - 'B'**

**Answer the following short-answer-type questions with word limit 150-200 : (3 5=15)**

- Q.1 Explain the forward and reverse biasing of a PN junction diode.

**OR**

Explain TIL in detail.

- Q.2 Define IC. What are active and passive components in any IC?

**OR**

Explain scale of integration in IC's in detail.

- Q.3 What are ASCII codes? Why are they frequently used?

**OR**

Explain 1's and 2's complements with example.

- Q.4 What are universal gates? Why they are called so? Explain with example.

**OR**

Write down basic laws of Boolean Algebra.

- Q.5 Explain Binary Half Adder with suitable diagrams.

**OR**

What are comparators? Explain any one with example.

(3)

Code No. : C-193

**Section - 'C'**

**Answer the following long-answer-type questions with word limit 300-350 : (5 5=25)**

- Q.1 How a transistor can be used as a switch? Explain with diagram.

**OR**

What are main logic families? Also write their characteristics.

- Q.2 Describe the Advantages and limitations of ICs in detail.

**OR**

Classify the ICs on the basis of (a) Structure (b) function describe each in brief.

- \* Q.3 (i) Subtract  $(1010)_2$  from  $(1101)_2$   
(ii) Multiply  $(1101)_2$  by  $(1100)_2$   
(iii) Perform  $(11001)_2 - (101)_2$   
(iv)  $(1111000)_2 = (?)_8$

**OR**

Explain any one error detection code with example.

- Q.4 Explain K-map with the help of examples.

**OR**

Describe the De-Morgan's Theorem. How it is useful? Give example.

- Q.5 Compare the combinational and sequential logic circuits in detail.

**OR**

Compare Encoder and Decoder.